


Lecture 2

niceguy

January 10, 2024

1 Parallel Plate Transmission Lines

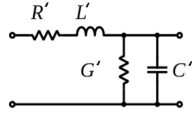We have shown that a parallel plate transmission line can be expressed as the following equivalent circuit.



Using KCL,

$$i(z, t) - i(z + \Delta z, t) = C' \Delta z \frac{\partial v(z + \Delta z, t)}{\partial t} + G' \Delta z v(z + \Delta z, t)$$

Dividing by Δz and taking the limit as it tends to zero,

$$-\frac{\partial i}{\partial z} = C' \frac{\partial v}{\partial t} + G' v$$

Similarly, for KVL,

$$-v(z, t) + i(z, t) R' \Delta z + L' \Delta z \frac{\partial i(z, t)}{\partial t} + v(z + \Delta z, t) = 0$$

and we get

$$\frac{\partial v}{\partial z} = -L' \frac{\partial i}{\partial t} - R' i$$

We solve this using phasors. Since we "inject" frequencies at the source, we can safely assume voltage and current are sinusoidal, with the same frequency. For

$$\begin{aligned} v(z, t) &= V_0 \cos(\omega t + \phi) \\ &= \Re\{V_0 e^{j(\omega t + \phi)}\} \\ &= \Re\{V_0 e^{j\phi} e^{j\omega t}\} \\ &= \Re\{\tilde{V}(z) e^{j\omega t}\} \end{aligned}$$

and similarly

$$i(z, t) = \Re\{\tilde{I}(z) e^{j\omega t}\}$$

We have now separated space- and time-dependent terms. this eventually gives

$$\begin{aligned} \frac{\partial \tilde{I}}{\partial z} &= -(G' + j\omega C') \tilde{V} \\ \frac{\partial \tilde{V}}{\partial z} &= -(R' + j\omega L') \tilde{I} \end{aligned}$$

Combining,

$$\begin{aligned} \frac{\partial^2 \tilde{V}}{\partial z^2} &= -(R' + j\omega L') \frac{\partial \tilde{I}}{\partial z} \\ &= (R' + j\omega L')(G' + j\omega C') \tilde{V} \\ &= \gamma^2 \tilde{V} \end{aligned}$$

where γ is as defined. It is a complex constant, with a real attenuation constant and imaginary phase constant.

Then the solution is

$$\tilde{V}(z) = V_0^+ e^{-\gamma z} + V_0^- e^{\gamma z}$$

and same for $\tilde{I}(z)$.

For a lossless transmission line, $R' = 0$, so

$$\gamma = j\omega \sqrt{L'C'}$$