

Lecture 11

niceguy

February 4, 2024

1 Smith Chart

Recall

$$Z(d) = Z_0 \frac{Z_L + jZ_0 \tan(\beta d)}{Z_0 + jZ_L \tan(\beta d)} = Z_0 \frac{1 + \Gamma_d}{1 - \Gamma_d}$$

where

$$\Gamma_d = \Gamma e^{-j2\beta d} = |\Gamma| e^{j(\theta_\Gamma - 2\beta d)}$$

where

$$\Gamma = Z_L - \frac{Z_0}{Z_L + Z_0}$$

Again, we can normalise this

$$z(d) = \frac{Z(d)}{Z_0} = \frac{1 + \Gamma_d}{1 - \Gamma_d}$$

and the same applies to resistance and reactance. Normalisation for admittance, conductance, and susceptance are obtained through dividing by Y_0 , so they are multiplicative inverses of impedance, etc., as one would expect. This gives

$$\Gamma_d = \frac{Z(d) - Z_0}{Z(d) + Z_0}$$

Let's say we are really messed up, and want to map (r, x) onto (Γ_r, Γ_i) . Then

$$\begin{aligned}
z &= \frac{1 + \Gamma_d}{1 - \Gamma_d} \\
r + jx &= \frac{1 + \Gamma_r + j\Gamma_i}{1 - \Gamma_r - j\Gamma_i} \\
&= \frac{(1 + \Gamma_r + j\Gamma_i)(1 - \Gamma_r + j\Gamma_i)}{(1 - \Gamma_r - j\Gamma_i)(1 - \Gamma_r + j\Gamma_i)} \\
&= \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2} + j \frac{2\Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2}
\end{aligned}$$

One can show that

$$\left(\Gamma_r - \frac{r}{r+1}\right)^2 + \Gamma_i^2 = \frac{1}{(1+r)^2}$$

1.1 r circles

This means for the same r , we have a circle centred at $(\frac{r}{r+1}, 0)$ with radius $\frac{1}{1+r}$. As $r \rightarrow \infty$, $\Gamma = 1$. This makes sense, because the reflection coefficient should tend to 1 as the load goes to infinity, i.e. open circuit. For a short circuit $r = 0$, we get a circle of radius 1 centred at the origin. No power is dissipated, so the reflection coefficient has to have a magnitude of 1.

1.2 x circles

We similarly have

$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x}\right)^2 = \frac{1}{x^2}$$

It is centred at $(1, \frac{1}{x})$ with radius $\frac{1}{|x|}$, so there is always a real Γ .