

# Lecture 3

niceguy

September 12, 2023

## 1 Instead of guessing...

Based on our current model, it is difficult to solve circuits with diodes, because we have to split into cases. Using a different model 1...

- $V$  and  $I$  have a nonlinear relation (one increases with the other)
- Until 0.7V is reached (for silicon), current is very low. This point is called the knee
- The region beyond 0.7V is called the forward bias
- At a negative voltage, there is a leakage current that is more or less constant,  $< 20\mu A$  for silicon
- At reverse breakdown voltage, there is an "avalanche" region, where current decreases (further from 0) rapidly

We approximate the relation with

$$I = I_S \left( e^{\frac{V}{V_T}} - 1 \right) \quad (1)$$

where  $I_S$  is the saturation or scaling current, and  $V_T$  the thermal voltage, where

$$V_T = \frac{k_B T}{q} \quad (2)$$

On the positive end, when  $V \gg V_T$ , we approximate

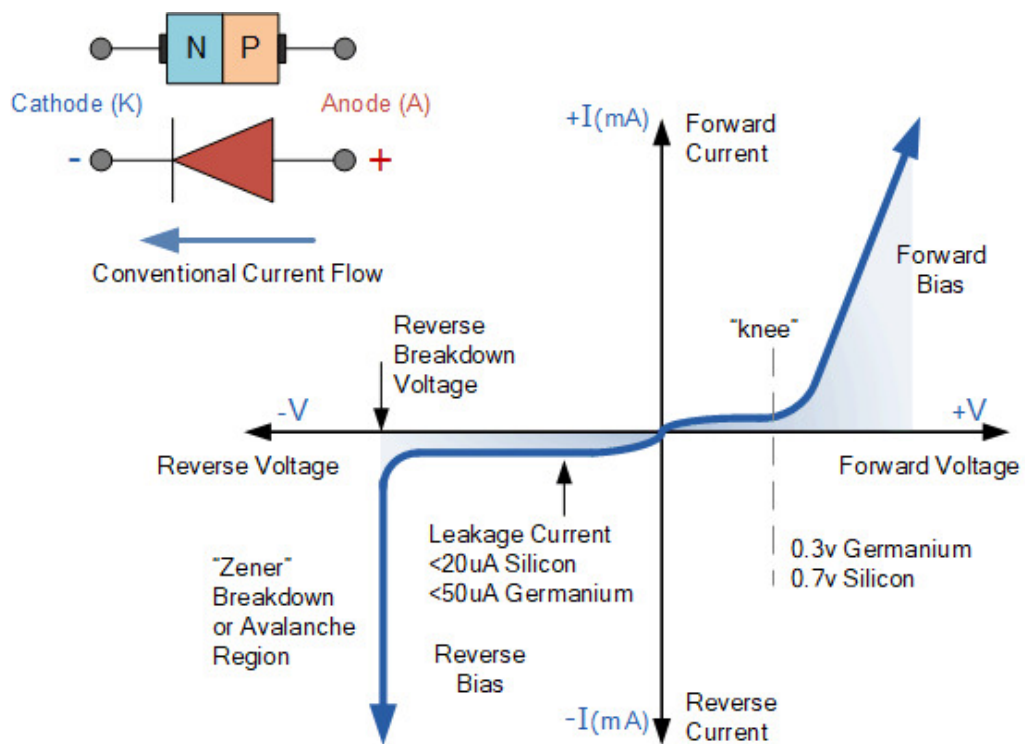


Figure 1: Forward and Negative Biases of Real Diodes

$$i \approx I_S e^{\frac{V}{V_T}} \quad (3)$$

*Note: we can of course use a Taylor approximation, but at small  $V$ , the diode is essentially off anyway.*

**Example 1.1.** Consider a simple circuit with a voltage source  $V_{DD}$ , resistor, and diode (forward bias). Current across diode is

$$I_D = I_S e^{\frac{V_D}{V_T}}$$

substituting into the resistor,

$$I_D = \frac{V_R}{R} = \frac{V_{DD} - V_D}{R}$$

Eliminating  $V_D$  gives the transcendental equation

$$I_D = \frac{V_{DD} - V_T \ln\left(\frac{I_D}{I_S}\right)}{R}$$

Inventing values and comparing it with the solution according to the first model

$$I_D = \frac{V_{DD}}{R}$$

We let the diode be 0.7V at 1mA and  $V_T$  be 25mV. Plugging, we find  $I_S = 6.9 \times 10^{-16}$ A. Solving gives us

$$I_D = 4.264\text{mA}, V_D = 0.736\text{V}$$